

① loop matrix or Tie set matrix

directed
loop


② cut set matrix.

③ incident matrix \rightarrow KVL

④ graph $\left\{ \begin{array}{l} \text{directed} \\ \text{undirected} \end{array} \right.$

\rightarrow node & branch

⑤ incident matrix:- [A]

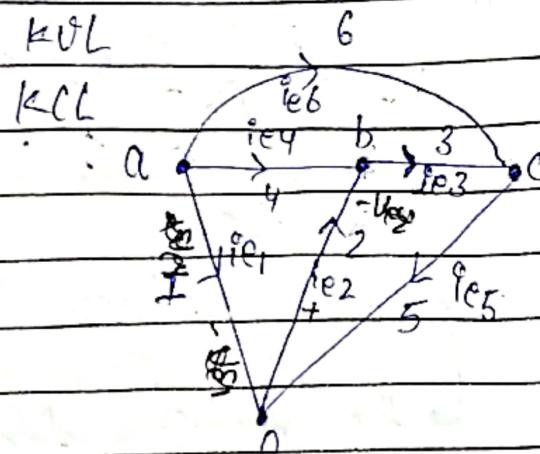

write KCL equation at node A, b, C and 0.

$$\text{at node A: } i_{e_1} + i_{e_4} + i_{e_6} = 0 \quad \rightarrow \textcircled{1}$$

$$\text{B: } i_{e_3} - i_{e_4} - i_{e_2} = 0 \quad \rightarrow \textcircled{2}$$

$$\text{C: } i_{e_5} - i_{e_6} - i_{e_3} = 0 \quad \rightarrow \textcircled{3}$$

$$0: \quad i_{e_2} - i_{e_2} - i_{e_5} \rightarrow \text{no new equation.}$$

it can be done

topological

from above
3 fundamental

\rightarrow now in topological form.

equation:-

$$\begin{matrix} & 1 & 2 & 3 & 4 & 5 & 6 & \rightarrow \\ \begin{matrix} a \\ b \\ c \\ 0 \end{matrix} & \left[\begin{matrix} 1 & 0 & 0 & 1 & 0 & 0 \\ 0 & -1 & 1 & -1 & 0 & 0 \\ 0 & 0 & 0 & 1 & -1 & 0 \\ 0 & 0 & -1 & 0 & 0 & -1 \end{matrix} \right] & \left[\begin{matrix} i_{e_1} \\ i_{e_2} \\ i_{e_3} \\ i_{e_4} \\ i_{e_5} \\ i_{e_6} \end{matrix} \right] & = & \left[\begin{matrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{matrix} \right] \end{matrix}$$

$$[A][i_e] = [0]$$

⑥ last row will be found using above

3 row hence it is simpler writing

• also sum of all four rows will be always zero.

So if you remove fourth row
then

$$[f_A] [f_e] = [f_o]$$

→ Induced Incident matrix.

↳ the matrix obtained from (A) by
eliminating one of the rows
is called R. Incidence matrix.



Suppression of reference node.

$$(A)_{n \times b} \quad (f_e)_{b \times 1} = (f_o)_{b \times 1}$$

n = no. of nodes.

b = no. of branch.

and for r.i.m \rightarrow isam ka yahi hai.

(A)

$(n-1) \times b$

EQU ① try to express the element voltage. In
term of node voltages (V_{AO}, V_{BO}, V_{CO})

$$V_{e1} = V_{AO}$$

$$V_{e2} = V_{OB} = -V_{BO}$$

$$V_{e3} = V_{BO} - V_{CO}$$

$$V_{e4} = V_{AO} - V_{BO}$$

$$V_{e5} = V_{CO}$$

$$V_{e6} = V_{AO} - V_{CO}$$

	V_{AO}	V_{BO}	V_{CO}	
V_{e1}	1	0	0	
V_{e2}	0	-1	0	V_{AO}
V_{e3}	0	1	-1	V_{BO}
V_{e4}	1	-1	0	V_{CO}
V_{e5}	0	0	1	
V_{e6}	1	-1	-1	

$$[V_{ei}] = [A]^T [V_n]$$

$b \times (n-1)$ node voltage

{0-reference
-ai}

① reduced ordered $[CA]^T$ matrix


$$[A] [C^0_e] = [0] \rightarrow ICCL$$

$$[A]^T [V_n] = [V_e] \rightarrow KV_L$$

T Loop & Branch.



⇒ Tie-set matrix / loop-incidence matrix
or Circuit matrix (B_a)

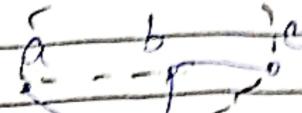graph → tree of graph.
e.g. 


- ① → tree is subset of the graph
Such that → all nodes will be present
→ no loops can be formed,
i.e. no closed path.
- ② → all nodes will be connected.

③ loop ⇒ branch of tree
 $t = (n-1)$

④ --- links → cut out branch on
co-tree.

⑤ branch of co-tree ↪

loop analysis → at a time

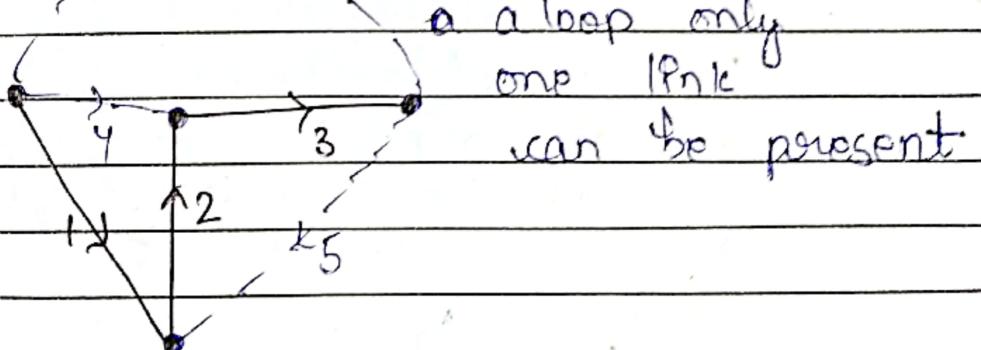

$$L4: e_4 - e_2 - e_1 = 0$$

$$L5: e_5 + e_2 + e_3 = 0$$


$$L6: e_6 - e_3 - e_2 - e_1 = 0$$

$$\begin{array}{c}
 \begin{matrix} & 1 & 2 & 3 & 4 & 5 & 6 \end{matrix} \\
 \begin{matrix} L_4 & -1 & -1 & 0 & +1 & 0 & 0 \end{matrix} \\
 \begin{matrix} L_5 & 0 & +1 & +1 & 0 & +1 & 0 \end{matrix} \\
 \begin{matrix} L_6 & -1 & -1 & -1 & 0 & 0 & +1 \end{matrix}
 \end{array}
 \left[\begin{array}{c} U_{e1} \\ U_{e2} \\ U_{e3} \\ U_{e4} \\ U_{e5} \\ U_{e6} \end{array} \right] = \left[\begin{array}{c} 0 \\ 0 \\ 0 \end{array} \right]$$

$$(B) [U_e] = [0] \leftarrow KVL$$

\downarrow
 $L_n \times b$

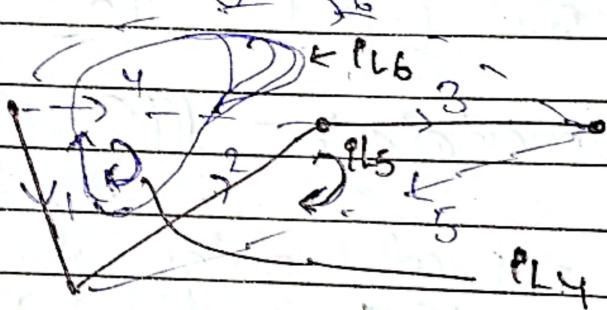\rightarrow KCL. Expressing elements current in term of loop current.



$$i_{e1} = -i_{L4} - i_{L6}$$

$$i_{e2} = i_{L3} + i_{L5} - i_{L4} - i_{L6}$$

$$i_{e3} = i_{L5} - i_{L6}$$

$$i_{e4} = i_{L4}$$

$$i_{e5} = i_{L5}$$

$$i_{e6} = i_{L6}$$

$$\begin{bmatrix} i_{e_1} \\ i_{e_2} \\ i_{e_3} \\ i_{e_4} \\ i_{e_5} \\ i_{e_6} \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & -1 & 0 & 0 \\ 0 & 1 & 0 & 0 & -1 & 0 \\ -1 & 0 & 1 & 0 & 0 & 0 \\ 0 & -1 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_{L_1} \\ i_{L_2} \\ i_{L_3} \\ i_{L_4} \\ i_{L_5} \\ i_{L_6} \end{bmatrix}$$

B_{X1}

$[B]$

no. of loop

B_{X1}

no. of loop
 χ_1

it is form of B of KVL


$$[B] [V_e] = [0] - \cancel{KCL} \text{ KVL}$$

$$[B]^T [i_L] = [V_e] - \cancel{KVL}$$


Cutset - matrin :- $\boxed{\text{CUTSET}} [Q]$

\rightarrow KCL not at nodes but at some line (Cut-set).

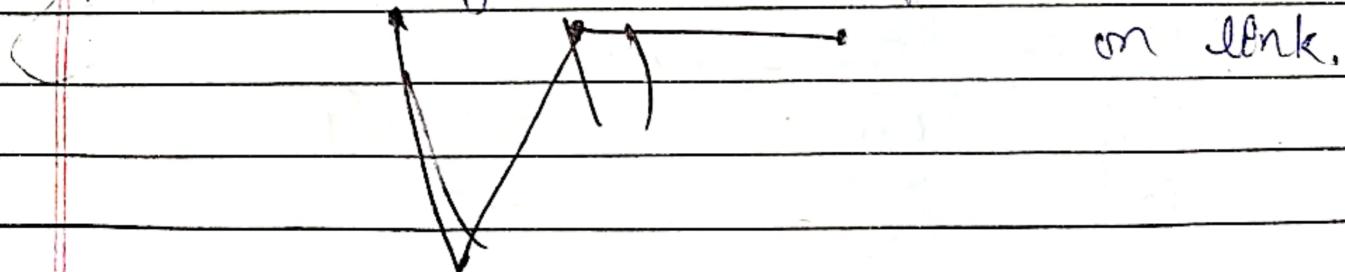Fundament cut-set \Rightarrow those line which break the network such that one side one node and one hole should be present and no limit



on link.

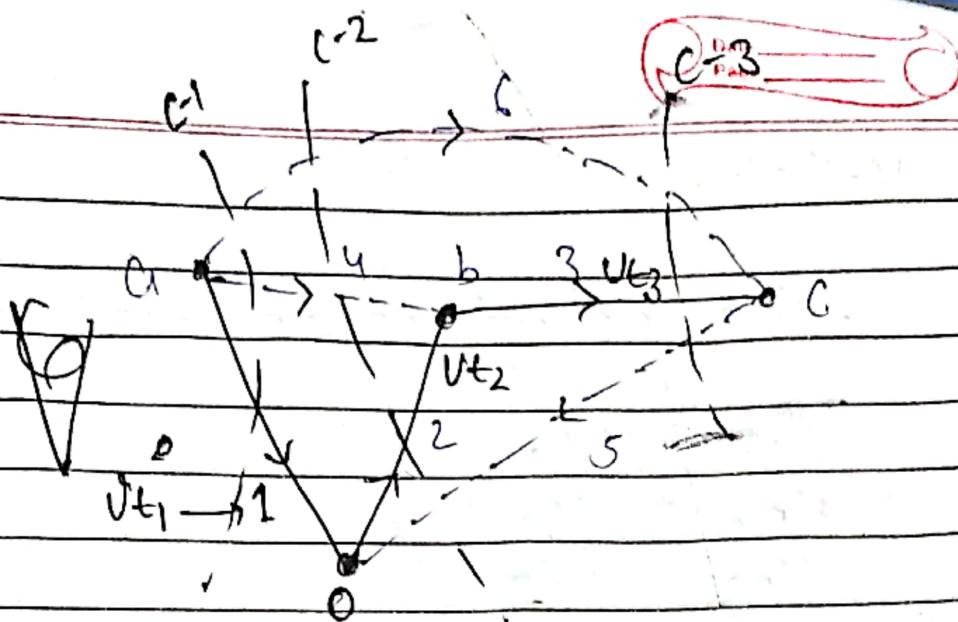

$$CS-1 \quad i_{e_1} + i_{e_2} + i_{e_3} = 0$$

$$CS-2 \quad i_{e_2} + i_{e_4} + i_{e_5} = 0$$

$$CS-3 \quad i_{e_3} - i_{e_5} + i_{e_6} = 0$$

	1	2	3	4	5	6	i_{e_1}	i_{e_2}	i_{e_3}	i_{e_4}	i_{e_5}	i_{e_6}
CS-1	1	0	0	1	0	1	1	0	1	0	0	0
CS-2	0	1	0	0	1	0	0	1	0	1	0	0
CS-3	0	0	1	0	-1	1	0	0	0	0	0	1

$$\begin{bmatrix} 0 \\ t \times n \end{bmatrix} \begin{bmatrix} i_e \\ n \times 1 \end{bmatrix} = \begin{bmatrix} 0 \\ t \times 1 \end{bmatrix}$$

$$t = n \tau$$

KCL-V-L.

update element voltage with node voltage.

$$V_{e_1} = V_{t_1}$$

$$V_{e_2} = V_{t_2}$$

$$V_{e_3} = V_{t_3}$$

$$V_{e_4} = V_{t_1} - (-V_{t_2}) = V_{t_1} + V_{t_2}$$

$$V_{e_5} = -V_{t_2} - V_{t_3}$$

$$V_{e_6} = V_{t_1} + V_{t_2} + V_{t_3}$$

$$\begin{matrix} & t_1 & t_2 & t_3 \\ \left[\begin{matrix} V_{e_1} \\ V_{e_2} \\ V_{e_3} \\ V_{e_4} \\ V_{e_5} \\ V_{e_6} \end{matrix} \right] & = & \left[\begin{matrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 1 & 0 \\ 0 & -1 & -1 \\ 1 & 1 & 1 \end{matrix} \right] & \left[\begin{matrix} V_{t_1} \\ V_{t_2} \\ V_{t_3} \end{matrix} \right] \end{matrix}$$

$$\left[\begin{matrix} V_e \\ B_{B1} \end{matrix} \right] = \left(\boldsymbol{\Omega}^{\Phi} \right)_{n \times n}^T \cdot \left[\begin{matrix} V_t \\ +x_1 \end{matrix} \right]$$